

MULTIMEDIA



UNIVERSITY

STUDENT ID NO

--	--	--	--	--	--	--	--	--	--

MULTIMEDIA UNIVERSITY

FINAL EXAMINATION

TRIMESTER 2, 2015/2016

EEN7046 – VLSI DESIGN

5 MARCH 2016
2.30 p.m - 5.30 p.m
(3 Hours)

INSTRUCTIONS TO STUDENTS

1. This Question paper consists of 6 pages with 4 Questions only.
2. Attempt **All** questions. All questions carry equal marks and the distribution of the marks for each question is given.
3. Please write all your answers in the Answer Booklet provided.

Question 1

- (a) Construct the truth table for the following functions.
 $F1(A, B, C, D) = \Sigma m(0, 2, 3, 5, 6, 7, 8, 10, 11, 14, 15)$
 $F2(A, B, C, D) = AB + \bar{C}D + A\bar{B}CD$

[8 marks]

- (b) Compute the simplified characteristic equations of the function in part (a).

[8 marks]

- (c) Design the functions in part (b) using programmable logic array.

[9 marks]

Continued ...

Question 2

- (a) Compute the equation of the output signal, F shown in Figure 2.

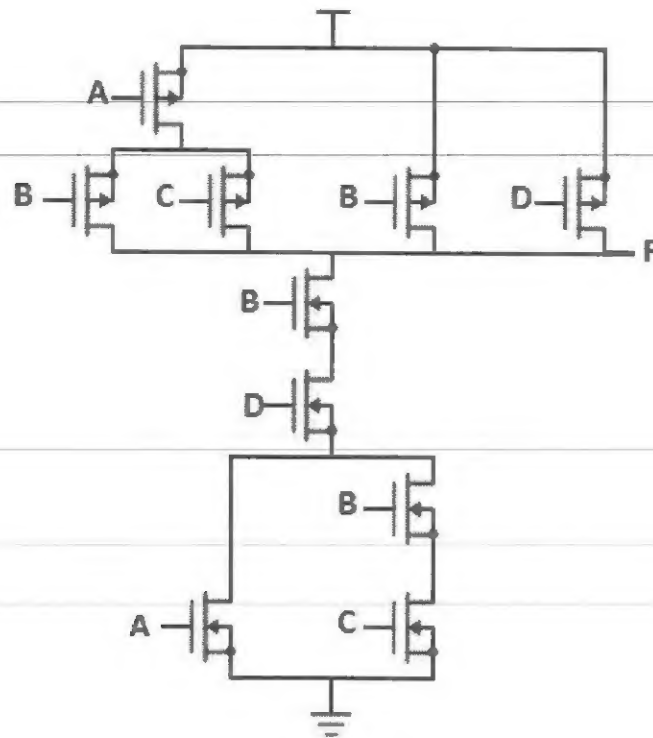


Figure 2

- [2 marks]
- (b) Compute the simplified characteristic equation of function F in part (a). [4 marks]
- (c) Implement the function F in part (b) using CMOS transistors. [8 marks]
- (d) Compute the W/L ratio of all the transistors used in the CMOS circuit that you draw in part (c) using $1\mu\text{m}$ CMOS technology. The transistor length must be minimum and the ratio of $\frac{[W/L]_p}{[W/L]_n} = 2$. [4 marks]
- (e) Design the function F in part (b) using pure NAND gates only. [7 marks]

Continued ...

Question 3

- (a) Answer the following questions regarding Early voltage, V_A in bipolar junction transistor (BJT).

- (i) Define Early voltage. [2 marks]
 (ii) Sketch I_C versus V_{CE} graph and identify the Early voltage in the graph. Write the collector current equation which contains Early voltage. [3 marks]

- (b) Fill up the comparison of voltage gain, current gain, input resistance and output resistance for the different configuration of BJT amplifiers given in Table 3(b).

[6 marks]

Table 3(b)

Configuration	Voltage gain	Current gain	Input resistance	Output resistance
Common emitter				
Emitter follower				
Common base				

- (c) A multistage source follower amplifier consists of NMOS transistors is shown in Figure 3(c). The transistors parameters are as follow.

$$K_{n1} = K_{n2} = 150 \mu A / V^2, V_{TH1} = V_{TH2} = 0.6 V, \lambda_1 = \lambda_2 = 0.$$

- (i) Given that $V_{DS2} = 4 V$. Determine the values for I_{D2} , V_{GS2} , V_{S1} , I_{D1} and V_{DS1} (by sequence). [8 marks]
 (ii) Determine V_{GS1} and V_{G1} . Given that $R_{in} = 200 k\Omega$. Find the appropriate values for resistor R_1 and R_2 . [6 marks]

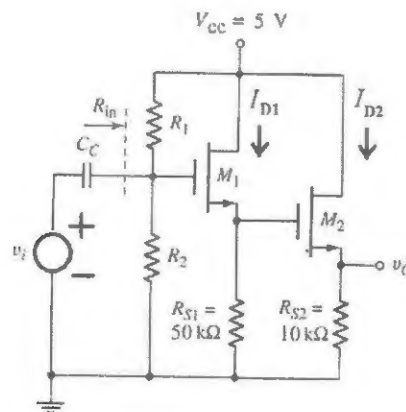
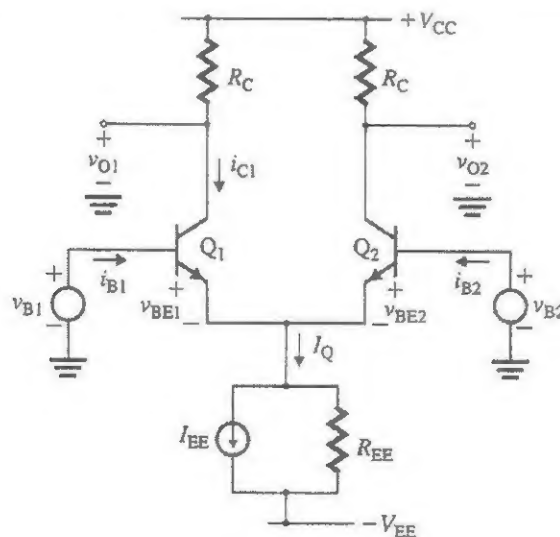


Figure 3(c)

Continued ...

Question 4

- (a) R-2R ladder is one of the most popular architecture of DAC architecture
- Sketch the circuit diagram of R-2R ladder DAC. [5 marks]
 - Describe the function of the circuit based on the circuit diagram in (a)(i) above. [4 marks]
 - Describe the advantage of R-2R ladder compared to weighted-resistor DAC. [2 marks]
 - Write down the V_{out} equation for R-2R ladder. Given that the reference voltage, V_{ref} for the 8-bit R-2R ladder is 3V. If $B_{in}=11100101$, determine the output voltage of the DAC. Also find V_{LSB} . [6 marks]
- (b) The emitter coupled pair shows in Figure 4(b) has $\beta=100$, $R_{EE}=50k\Omega$, $r_{\mu}=\infty$, $r_o=\infty$, $R_C=10k\Omega$, $I_Q=1mA$, $V_T=26mV$ and $V_{CC}=15V$. Assume that $i_{C1}=i_{C2}$.
- Determine g_m and r_{π} . [3 marks]
 - Find the differential-mode input impedance, R_{id} . [2 marks]
 - Determine the differential mode gain, A_d . [3 marks]

**Figure 4(b)****Continued ...**

Appendix: Useful formula

$$V_T = \frac{kT}{q}$$

$$I_B = \frac{I_C}{\beta_F}$$

$$I_E = \frac{-I_C}{\alpha_F}$$

$$I_C = I_S \left(\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{V_T}$$

$$C_b = \tau_F g_m$$

$$r_\pi = \frac{\beta}{g_m}$$

$$r_o = \frac{1}{\frac{\partial I_C}{\partial V_{CE}}} = \frac{V_A}{I_C}$$

$$r_\mu = \beta r_o$$

$$I_D = \frac{k'}{2} \left(\frac{W}{L} \right) [2(V_{GS} - V_t)V_{DS} - V_{DS}^2]$$

$$L_{eff} = L_{drawn} - 2L_D - X_d$$

$$V_A = V_M = L_{eff} \left(\frac{dX_d}{dV_{DS}} \right)^{-1} = \frac{1}{\lambda}$$

$$I_D = \frac{k'}{2} \left(\frac{W}{L_{eff}} \right) (V_{GS} - V_t)^2 \left(1 + \frac{V_{DS}}{V_A} \right)$$

$$r_o \text{ (BJT)} = 1/\eta g_m$$

$$\phi_f = \frac{kT}{q} \ln \left(\frac{N_A}{n_i} \right)$$

$$\gamma = \frac{\sqrt{2q\epsilon N_A}}{C_{ox}}$$

$$V_t = V_{to} + \gamma (\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f})$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

$$k' = \mu_n C_{ox}$$

$$V_{OV} = V_{GS} - V_t$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = k' \frac{W}{L} V_{OV}$$

$$C_{gs} = C_{gd} = \frac{C_{ox} WL}{2}$$

$$r_o = \frac{V_A}{I_D}$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}}$$

$$\frac{\partial V_t}{\partial V_{BS}} = \frac{-\gamma}{2\sqrt{2\phi_f + V_{SB}}} = -\chi$$

$$\chi = \frac{C_{js}}{C_{ox}} = \frac{g_{mb}}{g_m}$$

$$f_T = \frac{1.5\mu_n}{2\pi L^2} V_{OV}$$

$$f_T = \frac{2\mu_n}{2\pi W_B^2} V_T$$

$$I_D = I_t \frac{W}{L} \exp\left(\frac{V_{OV}}{nV_T}\right) \left[1 - \exp\left(\frac{-V_{DS}}{V_T}\right) \right]$$

End of Paper